

CONTENTS

CHAPTER	TITLE	PAGE NO.
1.	INTRODUCTION	1
2.	BACKGROUND DISCUSSION	5
2.1	The impedance of C & L	5
2.1.1	Equivalent ckt. for 'C'	7
2.2	Single frequency LCRQ meter	9
2.2.2	The series equivalent form	10
2.3.1	Data sheets MC1494L (XR-2208)	12
2.3.2	Operation Amplifier LM301A	18
2.3.3	Instrumentation Amplifier	19
2.3.4	Precision Voltage Regulator	20
2.3.5	A/D converter	20
2.3.6	Latches	21
2.3.7	Analog Switches	21
2.3.8	Function Generators	22
2.3.9	Current Sources	24
2.4	XASM85.COM	25
2.5	'C' calculation for ferroelectric materials	26
3.	MEASUREMENT SYSTEM HARDWARE	
3.1	Block Schematic of VLCRQ meter	34
3.2	Resistance measurement system	37
3.3	Voltage measurement system	41
3.4	Multichannel thermocouple system	44
3.5	A/D Converter system	48

3.6	Keyboard & display system	50
3.7	Capacitance measurement block schematic	53
3.8	Inductance Measurement system	72
4.	MEASUREMENT SYSTEM SOFTWARE	
4.1	Keyboard Interface	78
4.2	Key Entry flowchart	83
4.3	Voltage measurement software	83
4.4	Resistance measurement software	85
4.5	Capacitance measurement software	87
4.6	Display software	91
4.6.1	Display software for voltage & Resistance measurement	91
4.6.2	Display software for capacitance -tanδ measurement	92
	i] Capacitance Display	
	ii] Frequency Display	
	iii] Tanδ Display	
5.	PC ADD-ON	100
	Tends & comments	
6.	APPENDICES	140



- 1] Fig. 2.a Equivalent circuit model for (C&L); impedance Z
- 2] Fig. 2.b Parallel equivalent model for C
- 3] Fig. 2.c Series equivalent model for C
- 4] Fig. 2.1a Parallel equivalent model for L
- 5] Fig. 2.1b Series equivalent model for L
- 6] Fig. 2.2a Floating Load configuration using OPAMP
- 7] Fig. 2.2b BJT driver floating load configuration
- 8] Fig. 2.2c FET driver floating load configuration
- 9] Fig. 2.3a Phasor diagram for resistance
- 10] Fig. 2.3b Phasor diagram for capacitance
- 11] Fig. 2.3c Phasor diagram for inductance
- 12] Fig. 3.1 Block Diagram of VLCRQ meter
- 13] Fig. 3.2a Variable V to I switching circuit
- 14] Fig. 3.2b R-measurement circuit diagram
- 15] Fig. 3.3 V-measurement circuit diagram
- 16] Fig. 3.4a C-measurement circuit diagram
- 17] Fig. 3.4b Frequency dependent current source
- 18] Fig. 3.4c C-tan δ measurement circuit diagram
- 19] Fig. 3.4d Schematic diagram for XR-205
- 20] Fig. 3.5 A/D converter section
- 21] Fig. 3.6 Keyboard & Display controller

- Table - 2.1 Frequency versus impedance for various capacitances
- Table - 2.2 Frequency versus impedance for various inductances
- Table - 3.1 Function selection
- Table - 3.2a R-measurement source current, Vref. & Resistance
- Table - 3.2b R-measurement control format
- Table - 3.3 V-measurement control format containing gain & Vref.
- Table - 3.4 TC selection
- Table - 3.6a Table for permittivity, Disc dia.,disc.thick,capacita
- Table - 3.6b Fcount Vs Frange, width count=10
- Table - 3.6c Fcount Vs Frange, width count=10
- Table - 3.6d Table for freq. C,I,R & Vref.
- Table - 3.6e Control format, C-measurement
- Table - 4.1 Key codes
- Table - 4.2 Control port address
- Table - 4.3a ERROR Menu
- Table - 4.3b Indicator Menu
- Table - 4.3c Help-Menu
- Table - 4.4 D/A control format